
Lecture 8

Impedance

Copyright © 2015 by Mark Horowitz

Roadmap

In the last lecture we showed how we can represent a voltage waveform that changes in time another way – as a sum of tones (sinewaves). This representation contains the same information, just stored in a different way. These two representations are called transforms of each other.

This lecture will show you why this alternative representation is so useful. If you can represent an input as a sum of sinewaves, then it is very easy to compute the output of a circuit with resistors and capacitors. To show how this is done, we will introduce the concept of **impedance**, which is a generalization of resistance. Using impedance we can then estimate how the gain of circuit can change with frequency, creating **filters**, and how the response of these filters are graphed in a **Bode plot**.


Learning Objectives

-
- Learn what a dB is, and how it is used in voltage measurement
 - Logarithmic measure of gain (V_1/V_o)
 - 10 dB is a factor of 10 in power, 20 dB is a factor of 100
- Understand what a Bode plot is, and how to use it
 - It plots of circuit's gain in dB vs. log of the frequency
- Impedance is the relationship between voltage and current
 - For a sinusoidal input
 - $Z = V/i$, so for a capacitor $Z = \frac{1}{2\pi FC}$

CAPACITORS

Capacitors

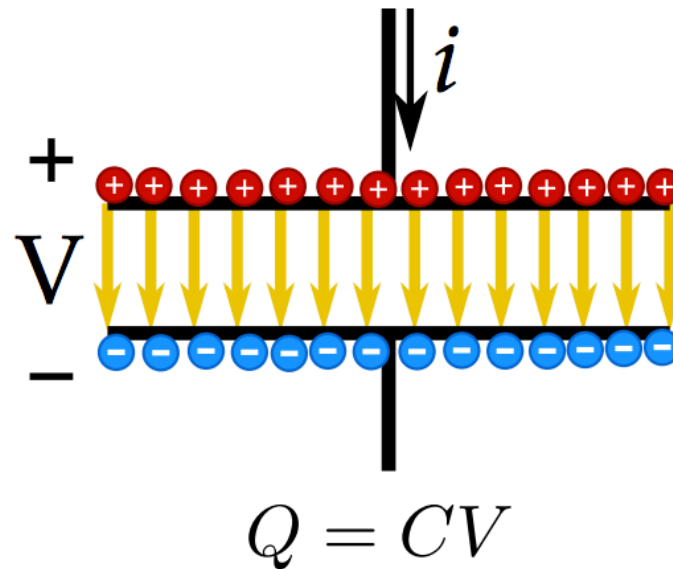
- Rather than relating i and V
 - $Q = CV$
 - Q in Coulombs
 - V in Volts
 - C in Farads
- Charge neutral
 - $+Q$ on one lead
 - $-Q$ on the other lead



iV for a Capacitor


- How do we relate I and V though?
 - $Q=CV$
 - $I = dQ/dt$
 - $dQ/dt = d(CV)/dt$
- $I = C dV/dt$
- Current = Rate of Voltage Change * Capacitance
 - If current is small, voltage changes a little bit
 - If current is large, voltage changes a lot

Capacitor Energy (Charging) – RC Circuit

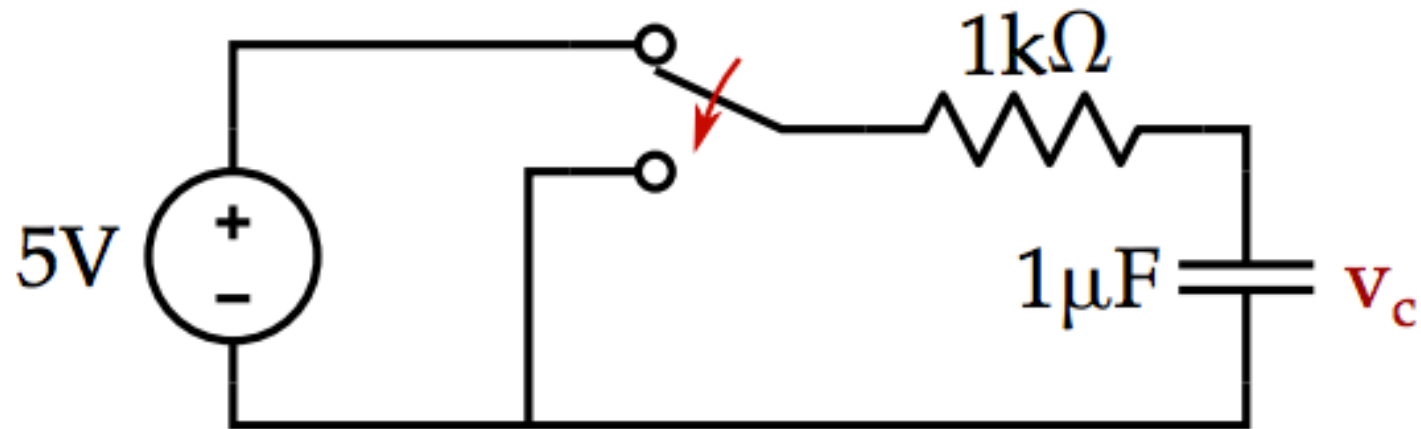

- Assume $V_c=0$ at $t=0$
- At $t=0$, switch flips up
- Plot V_c vs t

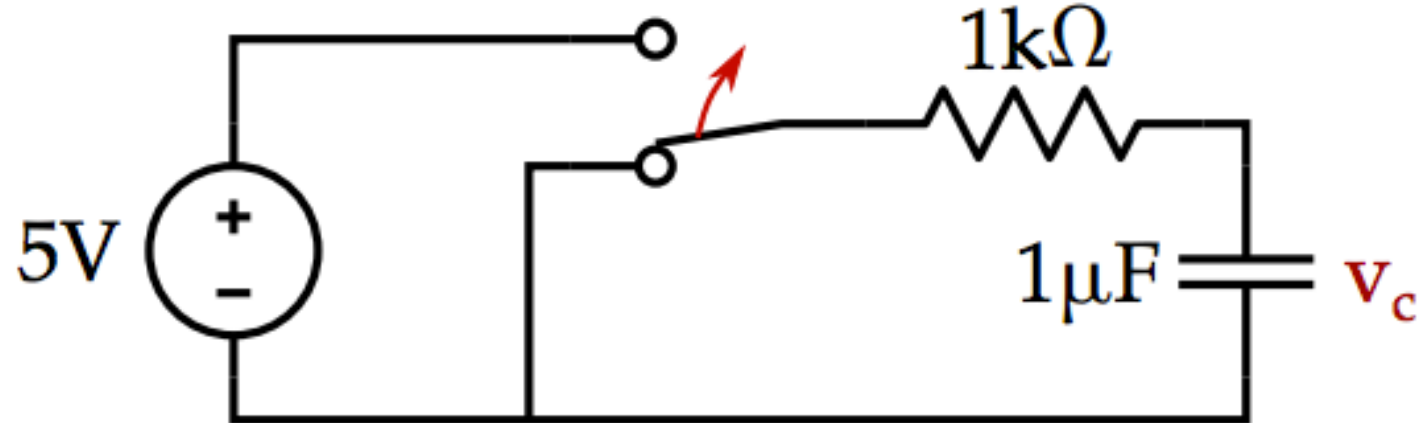Capacitor Energy (Discharging) – RC Circuit



- Assume $V_c=5V$ at $t=0$
- At $t=0$, switch flips down
- Plot V_c vs t

Key Ideas From The Last Lecture – RC Circuits

- When the input to the inverter is low, the output will be at V_{dd}
 - Right after the input rises, here is the circuit

- Want to find the capacitor voltage versus

- Just write the nodal equations:


- We just have one node voltage, V_{OUT}

- $i_{RES} = V_{out}/R_1$


- $i_{CAP} = CdV_{out}/dt$

- From KCL, the sum of the currents must be zero, so
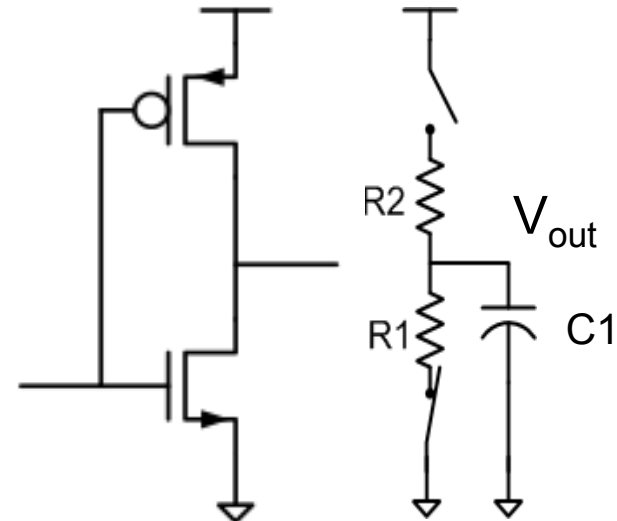
$$\frac{dV_{out}}{dt} = -\frac{V_{out}}{R_1 C}$$



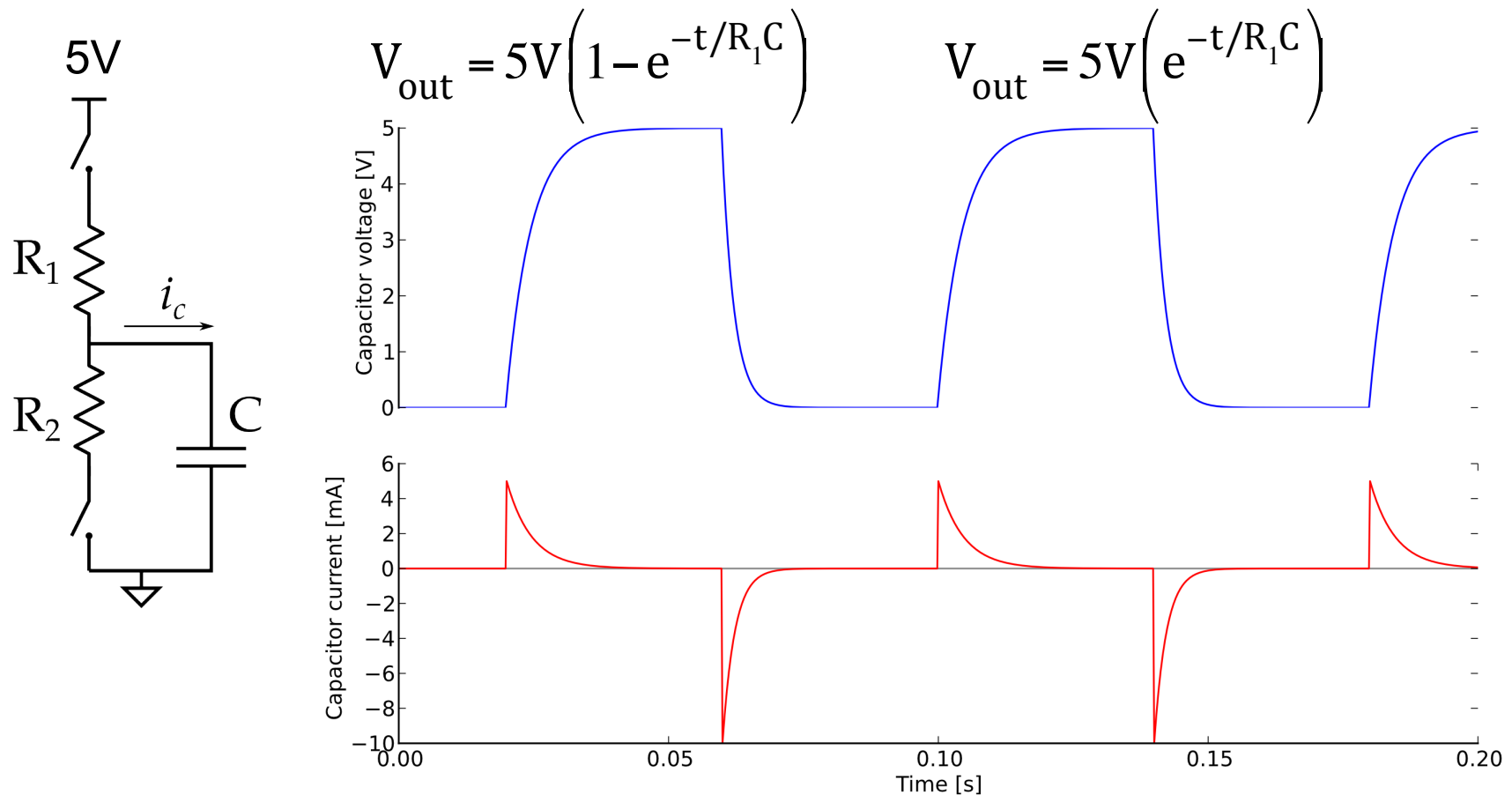Key Ideas From The Last Lecture – RC Circuits



In capacitor circuits, voltages change “slowly”, while currents can be instantaneous.

PREVIOUSLY IN E40M

IMPEDANCE


Impedance

-
- Ratio of the sine wave voltage across the device
 - To the sine wave current through the device
- For resistors
 - This is just the resistance, and doesn't depend on freq.
- For capacitors
 - This is a well defined quantity

$$Z = \frac{1}{2\pi F C}$$

- Which depends on the frequency of the sine wave

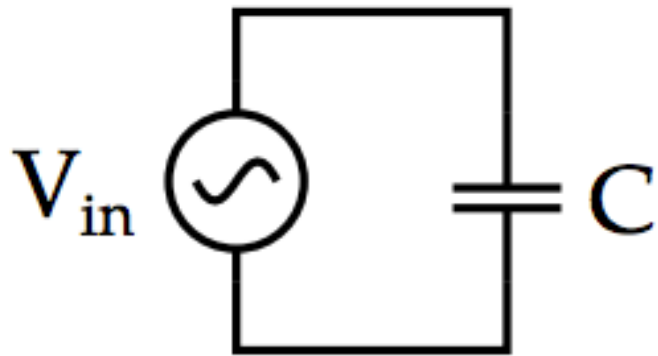
What happens when we put sine waves into a Capacitor?



- $V_{in} = \sin(2\pi f t)$
- $I_c = C \, dV_{in}/dt$
- $I_c = C \, 2\pi f \cos(2\pi f t)$
- $|Z| = V_{in}/I_c = 1/(2\pi f C)$

But How To Solve This Circuit?

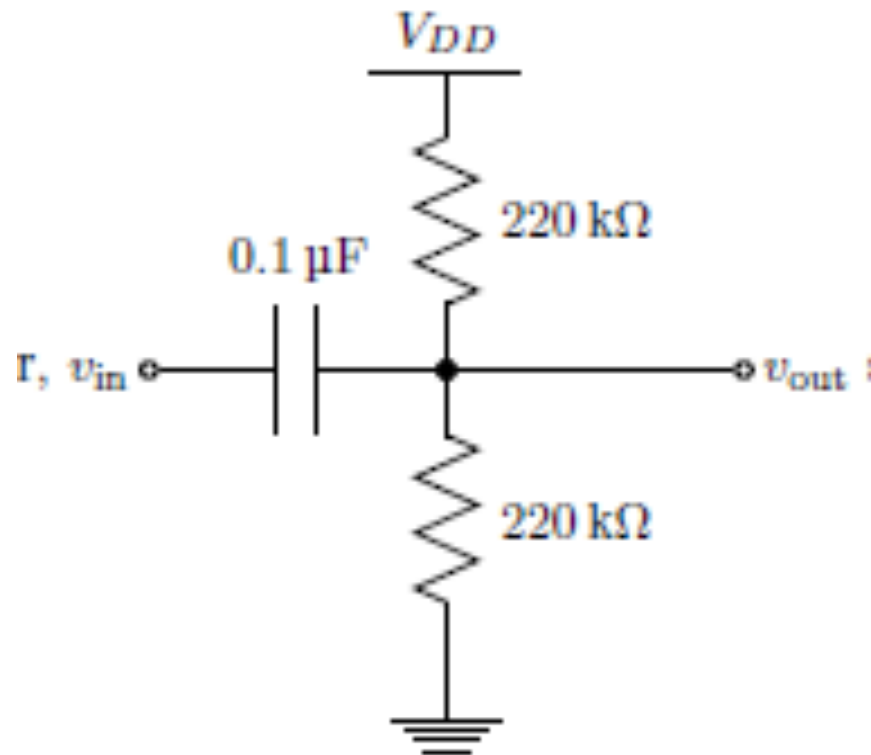- The input voltage is sound from your computer.
- Why do we need this circuit?




Superposition to the Rescue

- We know that sound can be represented by
 - A sum of sinewaves
- We also know that R, C are linear elements
 - So superposition holds
- Superposition says
 - The output is the sum of the response from each source
- So the output from a sound waveform
 - Is the sum of the outputs generated from each sinewave

Sinewave Driven Circuits


- All voltages and currents are sinusoidal
- So we really just need to figure out
 - What is the amplitude of the resulting sinewave
 - And sometimes we need the phase shift too (but not always)
- These values don't change with time
 - This problem is very similar to solving for DC voltages/currents
- In fact can solve it exactly the same way ...

RC Circuit Analysis Using Impedance

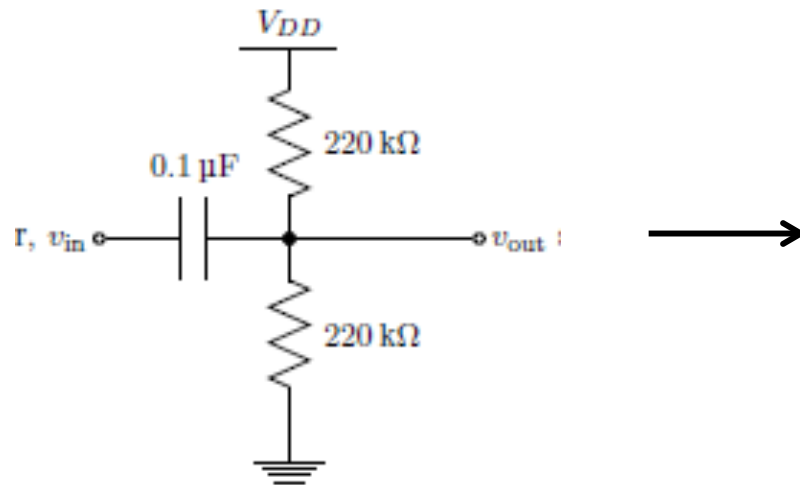

- The circuit becomes just a voltage divider, and we can analyze it the same way we have analyzed resistor only circuits.
 - That's the power of using impedance!

Analyzing RC Circuits Using Impedance

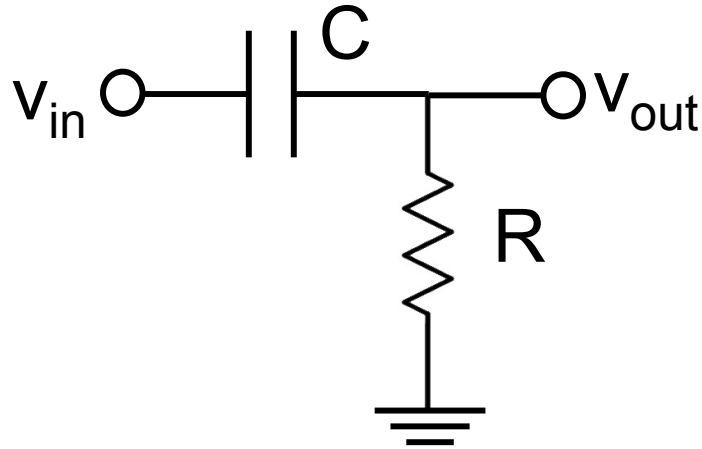

$$Z_C = \frac{1}{2\pi f C}$$


$$Z_R = R$$

- If the circuit had two resistors then we would know how to analyze it

$$\frac{V_{\text{out}}}{V_{\text{in}}} = \frac{R_2}{R_1 + R_2}$$

- What if we do the same thing but use impedances

Analyzing RC Circuits Using Impedance

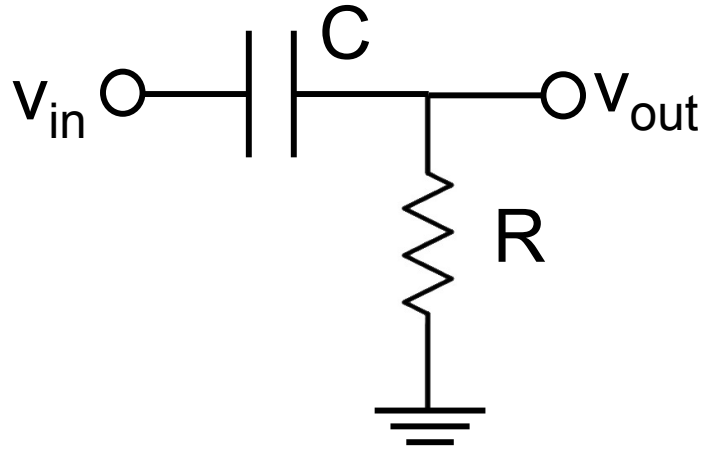

$$\frac{V_{out}}{V_{in}} = \frac{R}{R + \frac{1}{2\pi FC}} = \frac{2\pi FRC}{1 + 2\pi FRC}$$

- At low frequencies, ($F \approx 0$), $V_{out} = 0$ which means that low frequencies are not passed to the output. The capacitor blocks them.
 - Recall that we used this idea earlier to calculate the DC voltage at the output.
- At high frequencies (F large), $V_{out} = V_{in}$